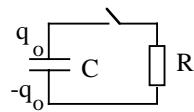



Notes on Inductance and Circuit Transients

Joe Wolfe, Physics UNSW

Circuits with R and C



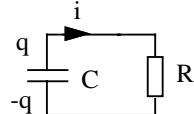What happens when you close the switch?
(close switch at $t = 0$)



Current flows *off* capacitor, so

$$i = - \frac{dq}{dt}$$

$$\text{Across capacitor: } V_C = \frac{q}{C} \quad C \equiv \frac{q}{V}$$

$$\text{Across resistor: } V_R = iR = V_c$$

$$\therefore \frac{dq}{dt} = -i$$

$$= -\frac{V}{R}$$

$$= -\frac{q}{RC}$$

$$\text{so } \frac{dq}{q} = -\frac{1}{RC} dt$$

$$\int \frac{dq}{q} = -\frac{1}{RC} \int dt$$

$$\ln q = -\frac{t}{RC} + \text{const.}$$

$$t = 0, q = q_0 \quad \therefore \ln q_0 = \text{const.}$$

$$\ln q - \ln q_0 = -\frac{t}{RC} \quad \ln a - \ln b = \ln \frac{a}{b}$$

$$\ln \frac{q}{q_0} = -\frac{t}{RC}$$

$$\therefore q = q_0 e^{-t/RC} \quad V = q/C \quad \therefore$$

$$V = V_0 e^{-t/RC} \quad (1)$$



$\tau = RC$ = time constant

$$\text{Units: } \Omega F = \frac{V}{A} \cdot \frac{C}{V} = \frac{s}{C} \cdot C = s$$

$$i = -\frac{dq}{dt}$$


$$= \frac{q_0}{RC} e^{-t/RC} = \frac{V_0}{R} e^{-t/RC}$$

$$i = i_0 e^{-t/\tau}$$

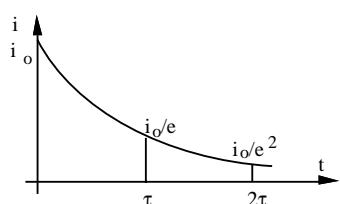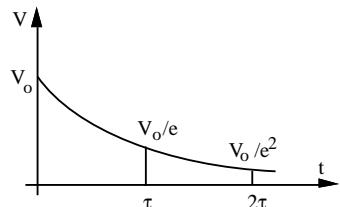

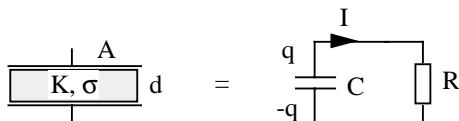Example

A real C uses dielectric with dielectric const. 4.0 and conductivity $\sigma = 2 \times 10^{-15} \Omega^{-1} m^{-1}$. It is charged then left disconnected for 1 hour. What fraction of charge remains? ($\sigma \equiv 1/\rho$)



$$C = \frac{\epsilon A}{d} = \frac{K\epsilon_0 A}{d}$$

$$R = \frac{\rho L}{A} = \frac{d}{A\sigma}$$


$$\therefore RC = \frac{d}{A\sigma} \cdot \frac{K\epsilon_0 A}{d} = \frac{K\epsilon_0}{\sigma}$$

$$= \frac{4.0 \times 8.9 \times 10^{-12} F m^{-1}}{2.0 \times 10^{-15} \Omega^{-1} m^{-1}} = 1.78 \times 10^4 s$$

$$V = V_o e^{-t/RC}$$

$$\frac{Q}{Q_o} = \frac{V}{V_o} = e^{-t/RC} = e^{-3600/\tau} = 0.82$$

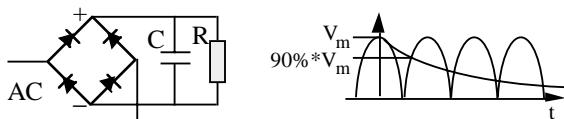Example Electronic appliance requires 20 W at 40 V DC, with max variation of 10%. What capacitance needed to store energy between cycles?



AC has 50 cycles per second, \therefore turns off 100 times/second, ie every 10 ms.

$$\frac{V}{V_m} = e^{-t/RC} \approx 0.90$$

$t = 10 \text{ ms}$, $C = ?$, what is R ?

R is the effective resistance of the circuit.

$$\text{We know } V \text{ and } P, \text{ so use } P = \frac{V^2}{R}$$

$$R = V^2/P = 80 \Omega.$$

$$e^{-t/RC} \approx 0.90$$

$$\frac{t}{RC} \approx -\ln(0.90)$$

$$\therefore C \approx \frac{-10 \text{ ms}}{80 \Omega * \ln 0.9}$$

$$= 13000 \mu\text{F}$$

Example the membrane of a "pacemaker" neurone of the heart has a capacitance of 10 pF and a conductance $G = 3.0 \text{ p}\Omega^{-1}$. Initially the potential difference across this membrane is -80 mV. The neurone begins a pulse when the potential difference reaches -60 mV. How long before it begins a pulse? Neglecting the duration of the electrical impulse itself, what is the pulse rate?

$$(1) \rightarrow \ln \frac{V}{V_o} = -\frac{t}{RC}$$

$$t = -RC \ln \frac{V}{V_o} = -\frac{10 \times 10^{-12}}{3 \times 10^{-12}} \ln \left(\frac{-60}{-80} \right)$$


$$= 0.96 \text{ s}$$

The "leakiness" of the membrane is now suddenly increased by a factor of 2. How long between electrical impulses? and what is the approximate pulse rate, again neglecting the duration of the individual impulses.


$$t = -R_2 C \ln \frac{V}{V_o} = -\frac{RC}{2} \ln \frac{V}{V_o} = \dots$$

$$= 0.48 \text{ s}$$

RC charging

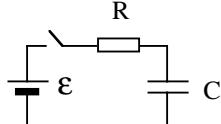

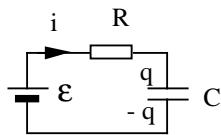What happens when you close the switch?
(close switch at $t = 0$,
 $q = 0, V = 0$)



Current flows onto capacitor, so

$$I = + \frac{dq}{dt}$$

Kirchoff $\mathbf{\Sigma} \mathbf{E} = iR + \frac{q}{C}$

take derivatives, use $i = + \frac{dq}{dt}$

$$\therefore 0 = R \frac{di}{dt} + \frac{i}{C}$$



rearrange: $\frac{di}{i} = - \frac{dt}{RC}$

$$\therefore \ln i = - \frac{t}{RC} + \text{const}$$

initial condition $\Rightarrow \ln i_0 = \text{const}$


$$i = i_0 e^{-t/\tau} = \frac{\mathbf{\Sigma} \mathbf{E}}{R} e^{-t/\tau} \quad (2)$$

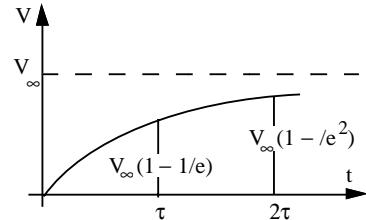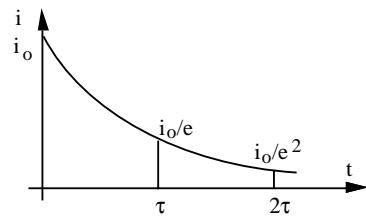where $i_0 = \mathbf{\Sigma} \mathbf{E}/R$ and $\tau = RC$



Inductance

Self-induction

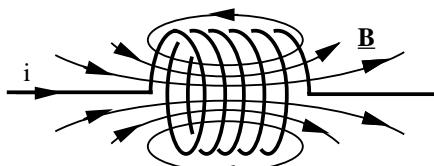

flux through each turn of coil $\approx \phi_B$

Faraday $\mathbf{\Sigma} \mathbf{E} = - \frac{d(N\phi_B)}{dt}$

Inductance, L $L \equiv \frac{N\Phi_B}{i}$ $\quad (3)$

(L is the total flux linkage per unit current)

$$\text{So } \mathbf{\Sigma} \mathbf{E} = - L \frac{di}{dt} \quad (4)$$


Note: $\mathbf{\Sigma} \mathbf{E}$ in coil \propto rate of change in i

cf V across C \propto integral of i


Units: 1 henry = 1 Volt second/amp

Lenz's law:

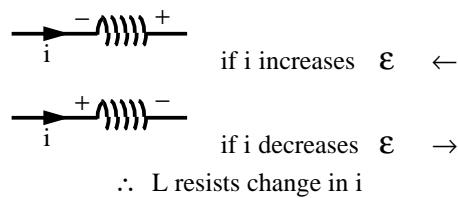\mathcal{E} acts in direction to maintain current (and $\therefore \mathbf{B}$)



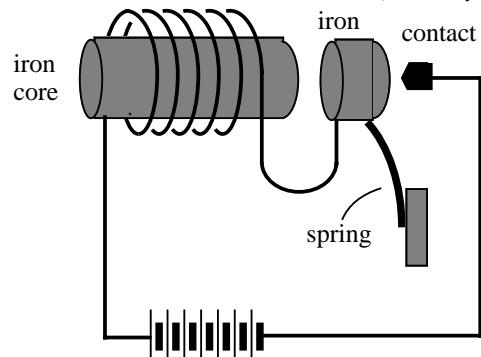
Example Automobile ignition coil (schematic)
(not in syllabus)



spring moves iron right to close contact. i flows which causes \mathbf{B}
 \mathbf{B} attracts iron to left, which opens circuit

$$\mathcal{E} = -L \frac{di}{dt} \quad i \rightarrow 0 \text{ quickly so large } \mathcal{E}$$

Ideal Solenoid

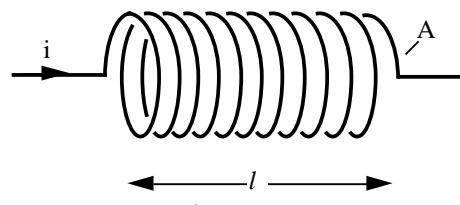

$$\begin{aligned} & n \text{ turns/m} \\ & N\Phi_B = n l B A \\ & \text{but } B = \mu_0 n i \\ \therefore L &= \frac{N\Phi_B}{i} = \frac{n l \mu_0 n i A}{i} \\ L &= \mu_0 n^2 l A \end{aligned} \quad (5)$$

Note: for non-magnetic materials, $\mu \approx \mu_0 = 4\pi 10^{-7} \text{ Hm}^{-1}$
magnetic materials, $\mu \gg \mu_0 \quad \therefore$ iron cores for large L .

Example Coil in kettle has $R = 60 \Omega$. It is 20 cm long, has 1 turn/mm, and is 4 mm in diameter.

- i) what is L ?
- ii) it is connected to 240 V_{rms}. Switch has breakdown potential of 1000 V and is turned off at peak of cycle ($V = 340$ V). Estimate the duration of spark. (Neglect other L).

$$\text{Peak } i = \frac{V_p}{R} = \frac{340}{60} = 5.7 \text{ A.}$$

$$\begin{aligned} (5) \rightarrow L &= \mu_0 n^2 l A \\ &= 4\pi 10^{-7} \cdot (10^3)^2 \cdot (0.2) \cdot \pi (2 \cdot 10^{-3})^2 \text{ SI} \\ &= 3.2 \mu\text{H.} \end{aligned}$$

$$\begin{aligned} \mathcal{E}_L &= -L \frac{di}{dt} \sim -1000 \text{ V during spark} \\ \therefore \frac{di}{dt} &\sim \text{const.} = \frac{1000 \text{ V}}{L} \\ \therefore \Delta t &\cong \frac{i}{\frac{di}{dt}} = \frac{5.7 \times 3.2 \cdot 10^{-6}}{1000 \text{ V}} = 18 \text{ ns.} \end{aligned}$$


(In practice Δt is larger because of other L 's.)

R - L Transients

Recall $\mathbf{\epsilon}_L = -L \frac{di}{dt}$ (Lenz's law: back emf)

This prevents sudden change in i ,

$\therefore i$ is continuous.

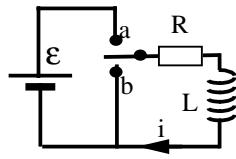

i) switch at a. After a long time,

$$\frac{di}{dt} = 0, \quad i = \mathbf{\epsilon}_c / R$$

ii) switch to b at $t = 0$

$$\therefore \text{at } t = 0, \quad i = \mathbf{\epsilon}_c / R$$



$$\text{Kirchoff: } -L \frac{di}{dt} = iR$$


$$\therefore \frac{di}{i} = -\frac{R}{L} dt$$

$$\int \rightarrow \therefore \ln i = -\frac{Rt}{L} + \ln i_0$$

$$\therefore i = i_0 e^{-Rt/L} = \frac{\mathbf{\epsilon}_c}{R} e^{-t/\tau}$$

$$\text{where } \tau = L/R \quad (6)$$
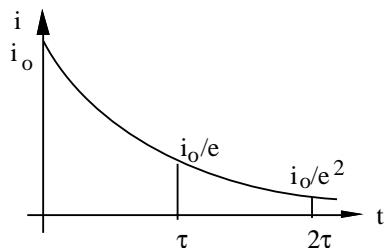
$$\text{Units: } \frac{H}{\Omega} = \frac{V}{A/s} \cdot \frac{A}{V} = s$$




iii) switch at b for long time ($i = 0$). Switch to a at $t' = 0$.


$$\mathbf{\epsilon}_c - L \frac{di}{dt} = iR$$

$$\text{solve} \rightarrow i = \frac{\mathbf{\epsilon}_c}{R} (1 - e^{-t'/\tau})$$

$$\text{where } \tau = L/R \quad (7)$$

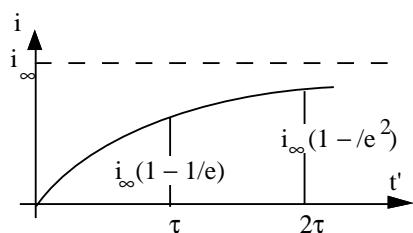

Example

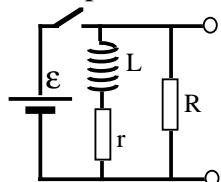

$$\mathbf{\epsilon} = 6V$$

$$L = 264 \text{ H}$$

$$r = 13k \ (\equiv 13 \text{ k}\Omega)$$

$$R = 47k$$

Switch closed for long time. Open at $t = 0$.


What does the CRO show?

Switch closed, after a long time $\frac{di}{dt} = 0$

Kirchoff's law: $V = i_1 r = i_2 R$

and $i_T = i_1 + i_2$



CRO shows $V = i_2 R = \mathbf{\epsilon} = 6 \text{ V}$

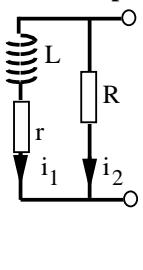Switch opened

L forbids abrupt change in i
 \therefore at $t = 0$ $i_1(0) = \mathcal{E}/r$
 $t \rightarrow \infty, i_1 \rightarrow 0$
 total series resistance is $r+R$
 so $i_1 = \left(\frac{\mathcal{E}}{r}\right) e^{-t(r+R)/L}$
 here $\tau = \frac{L}{r+R}$

$$i_2 = -i_1 \quad \text{so } V_{\text{CRO}} = i_2 R = -i_1 R = -\left(\frac{\mathcal{E}R}{r}\right)$$

$$V_{\text{CRO}} = -\left(\frac{\mathcal{E}R}{r}\right) e^{-t(r+R)/L}$$

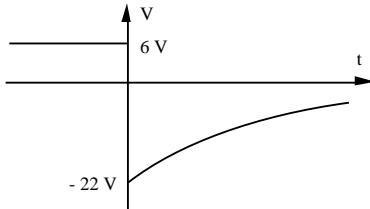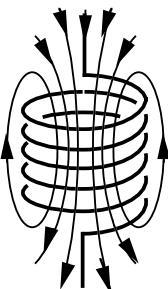**Energy in \tilde{B} of L**


Power supplied to L $= -\mathcal{E}_L i$
 i.e. $\frac{dU_B}{dt} = \left(L \frac{di}{dt}\right) i$
 $U_B = \int dU_B = \int_0^i L i' di'$
 $U_B = \frac{1}{2} L i^2 \quad (8)$
c.f. $U_E = \frac{1}{2} C V^2$

Energy density

$$\frac{U_B}{\text{vol}} = \frac{U_B}{Al} = \frac{\frac{1}{2} Li^2}{Al}$$
 $(5) \rightarrow L = \mu_0 n^2 l A \quad (5)$

(from mag.) $\rightarrow B = \mu_0 i n$

 $\therefore \frac{U_B}{\text{vol}} = \frac{1}{2} \frac{B^2}{\mu_0} \quad (9) \quad (\text{i.e. } U_E = \frac{1}{2} \epsilon_0 E^2)$

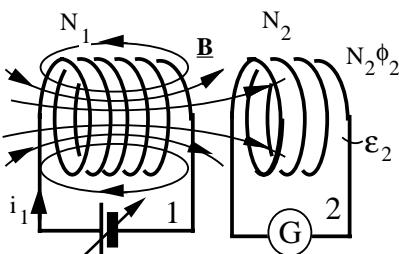Mutual Induction

Mutual Inductance M_{21} (of 2 w.r.t. 1)

$$M_{21} \equiv \frac{N_2 \Phi_{21}}{i_1} \quad (\text{i.e. } L = \frac{N \Phi}{i})$$

$$\text{so } M_{21} i_1 = N_2 \Phi_{21}$$


$$M_{21} \frac{di_1}{dt} = N_2 \frac{d\Phi_{21}}{dt} = -\mathcal{E}_2 \quad (\text{Faraday's law})$$

(long proof) $\Rightarrow M_{21} = M_{12} = M$

$$\text{so: } \mathcal{E}_2 = -M \frac{di_1}{dt}, \quad \mathcal{E}_1 = -M \frac{di_2}{dt} \quad (10)$$

(S.I. unit henry = Vs A⁻¹)

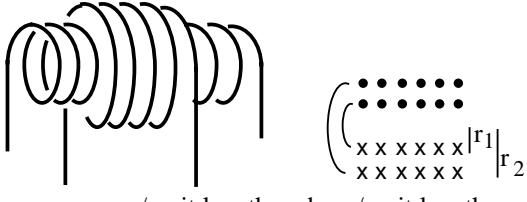Example Two long concentric solenoids. $M = ?$



n_1 / unit length and n_2 / unit length

$$M = M_{21} = \frac{N_2 \Phi_{21}}{i_1} = \frac{n_2 l \Phi_{21}}{i_1}$$

$$B_1 = \mu_0 i_1 n_1 \text{ and } \Phi_{21} = B_1 A_2$$

$$\therefore M = \frac{n_2 l}{i_1} (\mu_0 i_1 n_1) \pi R_2^2$$

$$M = \pi R_2^2 l \mu_0 n_1 n_2 \quad (11)$$

LC oscillations (assume ideal L: $r_L = 0$, ideal C: $r_C = \infty$)

Kirchoff's law:

$$-L \frac{di}{dt} = \frac{q}{C}$$

$$i = \frac{dq}{dt}, \text{ so } -L \frac{d^2i}{dt^2} = \frac{1}{C} \frac{dq}{dt} = \frac{i}{C}$$

$$\therefore \frac{d^2i}{dt^2} = -\frac{1}{LC} i = -\omega^2 i \quad \text{say}$$

solve: $i = \text{const sin}(\omega t + \text{const})$

$$i = i_m \sin(\omega t + \phi)$$

$$\text{where } \omega = \sqrt{\frac{1}{LC}} \quad (12)$$

$$V = -L \frac{di}{dt} = -L \omega i_m \cos(\omega t + \phi)$$

$$V = -V_m \cos(\omega t + \phi)$$

Energy

$$U_E = \frac{1}{2} CV^2 = \frac{C}{2} [....\cos....]^2$$

$$U_B = \frac{1}{2} Li^2 = \frac{L}{2} [....\sin....]^2$$

$$\begin{aligned} U_T &= U_E + U_B \\ &= \frac{1}{2} i_m^2 L [LC \omega^2 \cos^2(\phi) + \sin^2(\phi)] \\ &= \frac{1}{2} i_m^2 L \quad [= \text{constant}] \end{aligned}$$

also $V_m = i_m \omega L$

$$\text{so } U_T = \frac{1}{2} \frac{V_m^2}{\omega^2 L^2} L = \frac{1}{2} C V_m^2$$

Example Front end of a radio: $C_{\max} = C_{\min} = 1.1 \text{ pF}$

$$C_{\max} (3 \text{ in } //) = 3 \left(\frac{\epsilon_0 A}{d} \right) = 3 \frac{\epsilon_0 \pi r^2}{d} = \dots = 16.7 \text{ pF}$$

ii) If we want to tune the AM band (54 - 160 kHz) what values of L and C? How do we make the L?

$$f_{\max} = \frac{1}{2\pi} \omega_{\max} = \frac{1}{2\pi} \sqrt{\frac{1}{L(C_{\min} + C_1)}} \quad f_{\min} = \frac{1}{2\pi} \sqrt{\frac{1}{L(C_{\max} + C_1)}}$$

$$\therefore \frac{f_{\max}^2}{f_{\min}^2} = \dots = \frac{C_{\max} + C_1}{C_{\min} + C_1}$$

$$\therefore C_1 (f_{\max}^2 - f_{\min}^2) = C_{\max} f_{\min}^2 - C_{\min} f_{\max}^2$$

$$\therefore C_1 = \dots = 0.9 \text{ pF}$$

$$\begin{aligned} f &= \frac{1}{2\pi} \sqrt{\frac{1}{LC}} \quad \therefore L = \frac{1}{C} \cdot \frac{1}{4\pi^2 f^2} = \frac{1}{C_{\max} + C_1} \cdot \frac{1}{4\pi^2 f_{\min}^2} \\ &= 490 \text{ mH} \end{aligned}$$

$$(5) L = \mu_0 n^2 l A \quad \text{say } n = 2000/\text{m}, A = 5 \text{ cm}^2, l = ? \quad l = \frac{L}{\mu_0 n^2 A} = 200 \text{ m. Oops, try iron core: } \mu_r = \frac{\mu}{\mu_0} \sim 2000$$